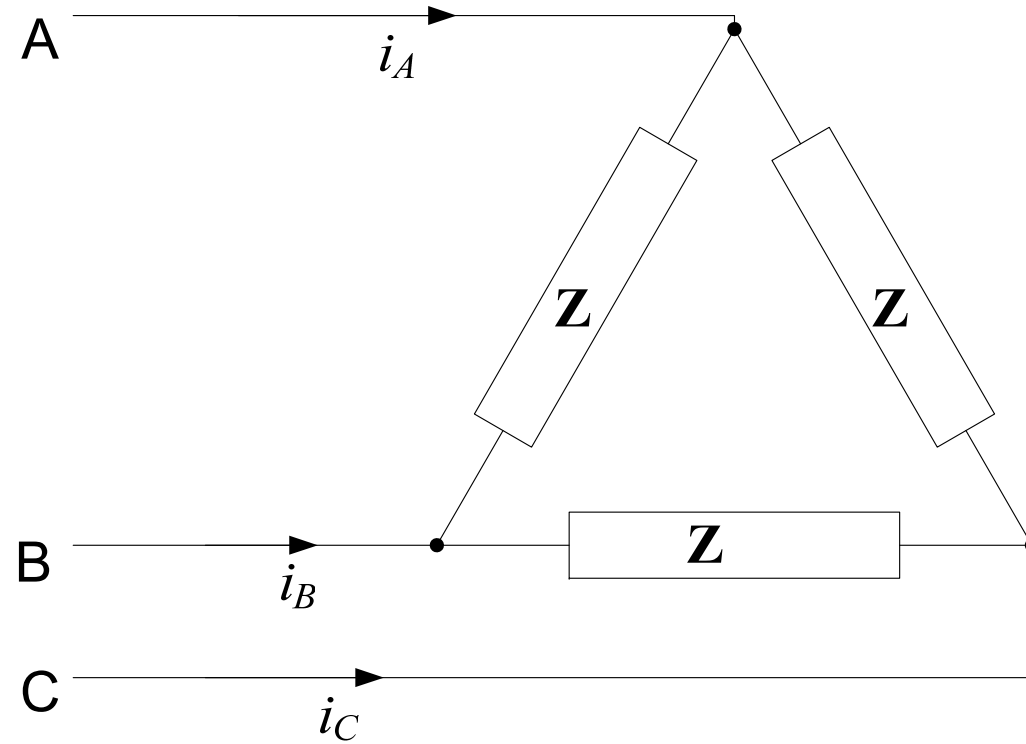


1. A three-phase, three-wire, ABC system, with an effective line voltage of $100\sqrt{3}$ V, has three impedances of Z in a Δ -connection. Determine the line currents (i_A , i_B , i_C) magnitude and phase angle for $Z = 5 \angle 45^\circ \Omega$, $V_{AB} = 100\sqrt{3} \angle 120^\circ$ V, $V_{BC} = 100\sqrt{3} \angle 0^\circ$ V, $V_{CA} = 100\sqrt{3} \angle 240^\circ$ V



2. Find a single equivalent Δ -connected load $\mathbf{Z_D}$ for the following circuit with $\mathbf{Z_d} = 40 + 40j \, \Omega$ $\mathbf{Z_Y} = 10 - 10j \, \Omega$.

